



## Introduction

In this experiment we are going to study:

1. The relationship between output voltage and input voltage (DC voltage limitation with z-diode)
2. The relationship between Z current and input voltage (DC voltage limitation with z-diode)
3. Measure the effects of load current  $I_L$
4. Study the AC voltage limiting and overvoltage protection with Z-diode
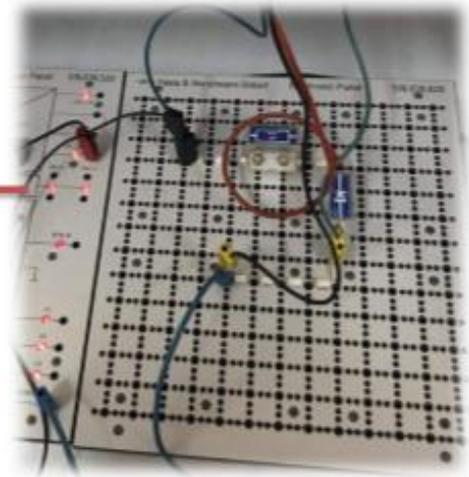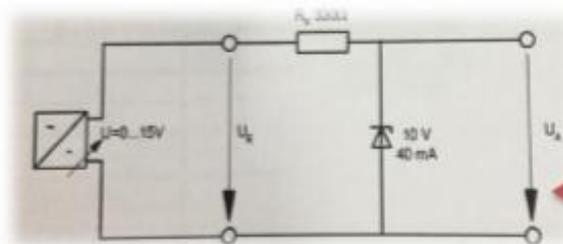
## Procedure:


- **Part one**(the relationship between  $U_s$  and  $U_A$ )
  1. Connect the circuit as shown.



2. Display DC voltage {0-15} volt across the circuit
3. Measure the voltage across the diode(see the attached table)
- 4.

$U_S$ v	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
$U_A$ v	0	1.06	2.08	3	3.95	4.9	6	7	8.01	9	10	10	10	10	10	10

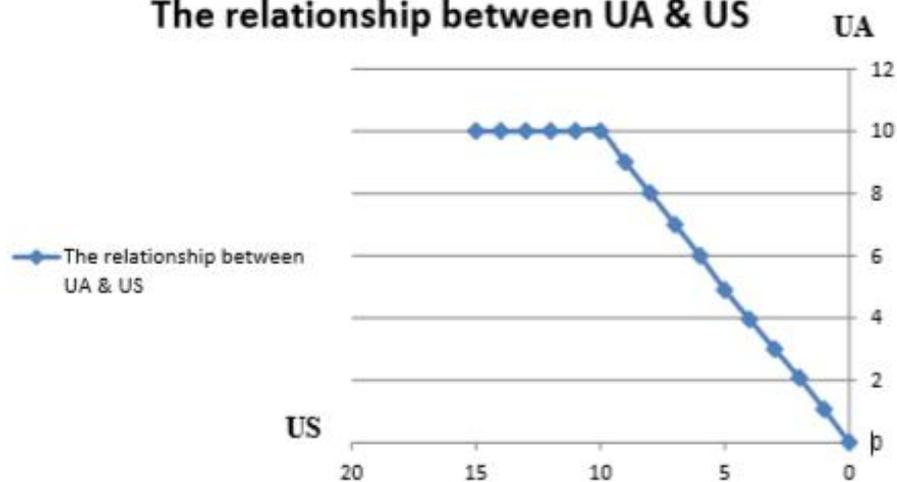
The relationship between  $U_A$  &  $U_S$



**Part Two**((the relationship between  $I_Z$  and  $U_Z$ )


**Procedure:**

1. We connected the circuit as shown

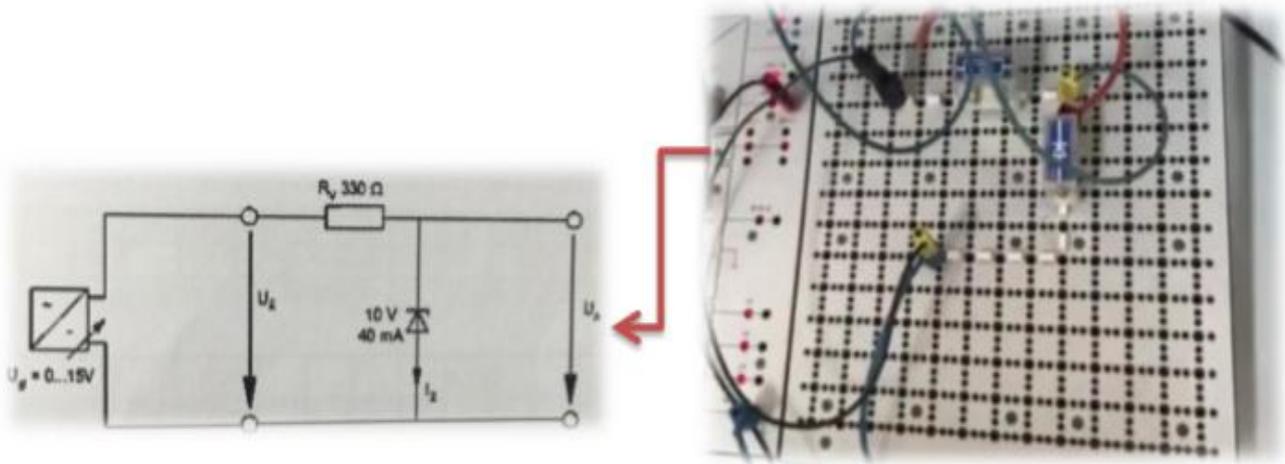



2. Display DC voltage {0-15} volt across the circuit
3. Measure the current through the diode.(see the attached table)

$U_Z$	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
$I_Z$	0	0	0	0	0	0	0	0	0	0	0	2.8	6.3	8.9	11.6	14.8

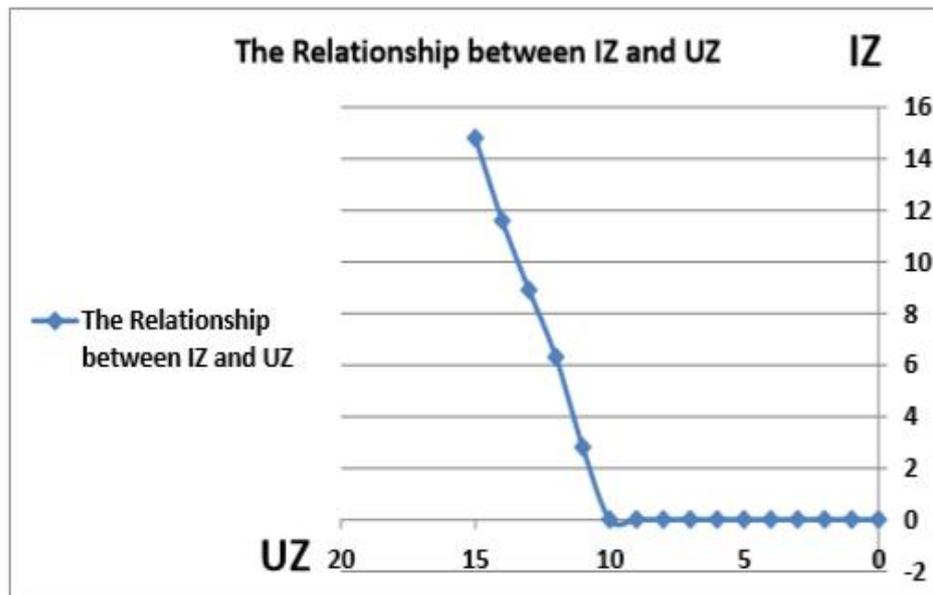


**Part three** (measure the effects of load current  $I_L$ )

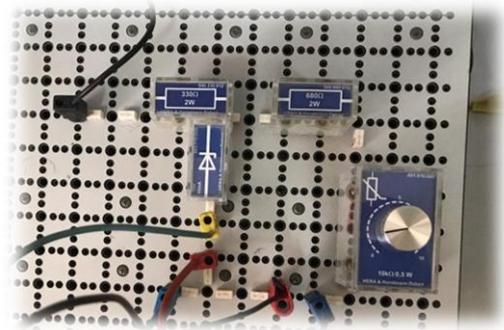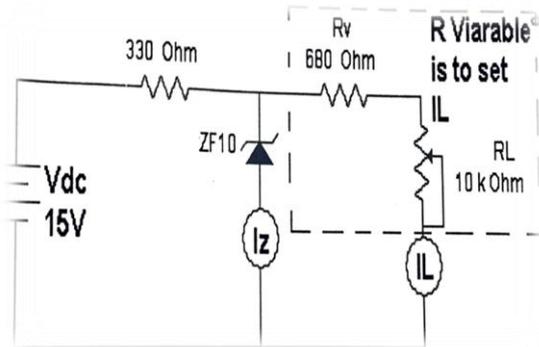Here we are going to control the current going through the  $R_L$  and examine the  $I_Z$  and  $I_L$  of the circuit, using the variable resistor, as the  $I_L$  increases through using the variable resistor.



$I_L$	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
$I_Z$	26.8	25.4	24.6	23.6	22.6	21.7	20.7	19.8	18.8	17.7	16.5	15.7	14.5	13.7	12.7	11.9

The relationship between ( $I_L$ -  $I_Z$ ).

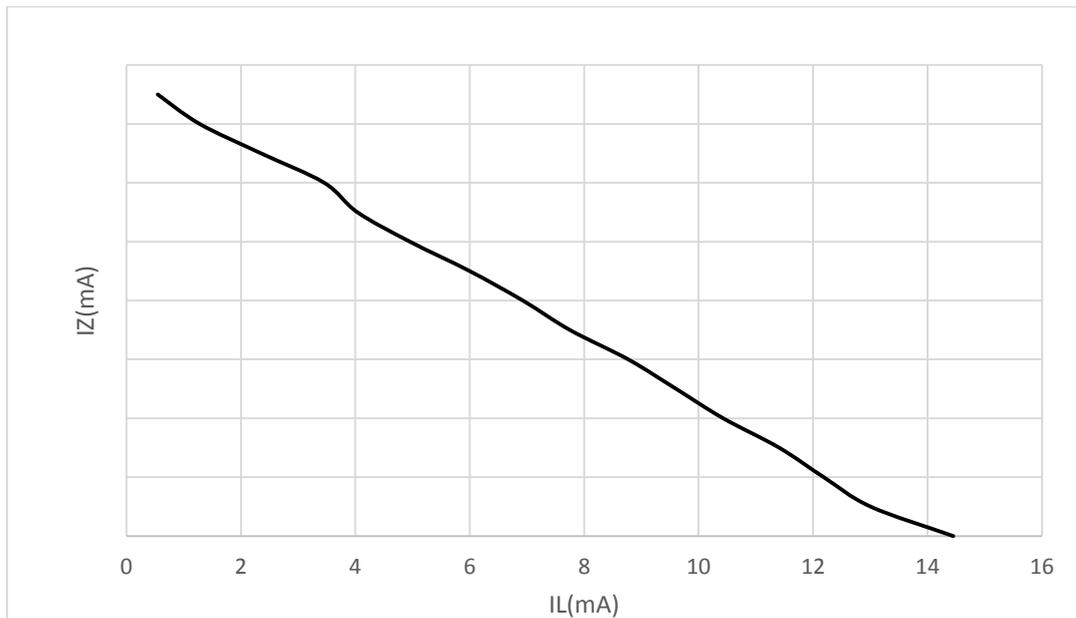

**Test 1:** What condition is needed that the output voltage remains constant in a limiter circuit with Z-Diode?

Answer:  $V_s > V_z$

**Test 2:** When does  $I_Z$  flow?



Answer:  $V_s > V_z$

**Test 3:** Under which condition is the limiting effect maintained although under load?

Answer:  $V_s > V_z$

*Part four (Voltage limiting and overvoltage protection with Z-diodes)*

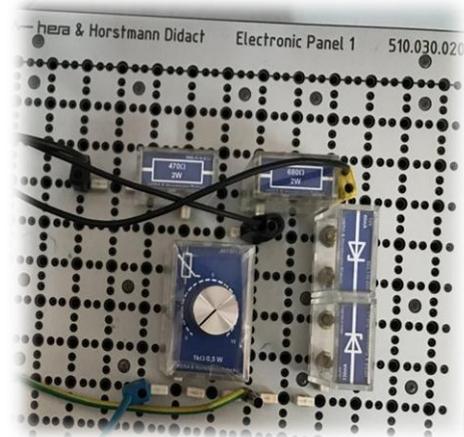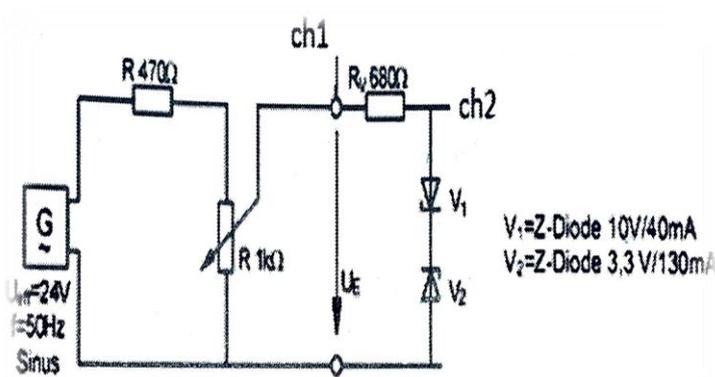The **Diode Clipper**, also known as a Diode Limiter, is a wave shaping circuit that takes an input waveform and clips or cuts off its top half, bottom half or both halves together to produce an output waveform that resembles a flattened version of the input. For example, the half-wave rectifier is a clipper circuit, since all voltages below zero are eliminated.




We connect the circuit as shown :

V1=Z diode 10V/40mA

V2=Z-diode 3.3V/130 mA

So when  $U_{eff}=10$  volt

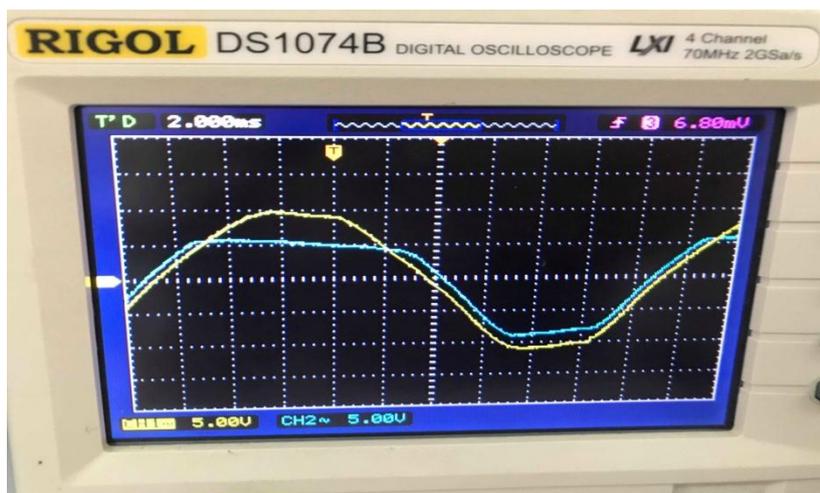

- The positive side cut at 4 volt ( $10-0.7-3.3=4v$ )
- The negative side cut at 10.7v

Now when the  $U_{eff} = 2\text{ V}$



Where the  $U_{eff}$  less than the  $V_z$  the zener doesn't work (still full wave.)

- Do you know the application possibilities for a Z-diodes?  
**Answer:** a zener diode can work as a voltage regulator to protect loads from getting defected by unregulated voltage, it can also be a waveform clipper.
- State the advantage of two opposed directed Z-diodes?  
**Answer:** one of them for forward . the other will be reverse

### Conclusion

Were able to understand the main role of the zener diode as a voltage regulator which is a Zener diode can be applied to a circuit to regulate the voltage applied to a load, as waveform clipper which is The output waveform will be clipped at the zener voltage plus the 0.7V forward volt drop of the other diode and as a voltage shifter as it can be applied to a circuit with a resistor to act as a voltage shifter. This circuit lowers the input voltage by a quantity that is equal to the Zener diode's breakdown voltage.

